



**EC310: Testing and Diagnosis  
of Digital System Design**

## **2020 Even Semester Project**

Hardware Design of  
Booth's Multiplier  
circuit  
with  
Built-in Self-Test  
Feature

**Prepared for:**

Ms. Kriti Suneja  
Assistant Professor,  
Dept. of ECE, DTU

**Prepared by:**

Abhishek Chaurasia	(2K17/EE/08)
Abhishek Choudhary	(2K17/EE/09)
Animesh Kulshreshtha	(2K17/EE/38)
Avisekh Ghosh	(2K17/EE/62)

## ABSTRACT


Very Large-Scale Integration (VLSI) has made a dramatic impact on the growth of integrated circuit technology. It has not only reduced the size and the cost but also increased the complexity of the circuits. The positive improvements have resulted in significant performance/cost advantages in VLSI systems.

There are, however, potential problems which may retard the effective use and growth of future VLSI technology. Among these is the problem of circuit testing, which becomes increasingly difficult as the scale of integration grows. Because of the high device counts and limited input/output access that characterize VLSI circuits, conventional testing approaches are often ineffective and insufficient for VLSI circuits.

Built-in self-test (BIST) is a commonly used design technique that allows a circuit to test itself. BIST has gained popularity as an effective solution over circuit test cost, test quality and test reuse problems. In this paper we are presenting implementation of BIST on Booth's Multiplier.

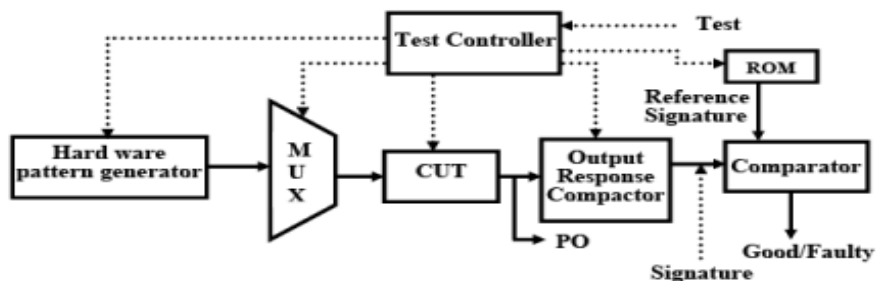
## Built-in Self-Test

Built-in Self-Test (or BIST) is a DFT technique in which testing is accomplished through built in hardware. The basic idea is to have a VLSI chip that tests itself. BIST is a design-for-testability technique that places the testing functions physically with the circuit under test (CUT). The basic BIST architecture requires the addition of three hardware blocks to a digital circuit: a test pattern generator, a response analyser, and a test controller. The test pattern generator generates the test patterns for the CUT. Examples of pattern generators are a ROM with stored patterns, a counter, and a linear feedback shift register (LFSR). A typical response analyser is a comparator with stored responses or an LFSR used as a signature analyser. It compacts and analyses the test responses to determine correctness of the CUT. A test control block is necessary to activate the test and analyse the responses. However, in general, several test-related functions can be executed through a test controller circuit.


 
## LFSR: Linear Feedback Shift Register

The LFSR is just a register formed from standard flip-flops, with the outputs of selected flip-flops being fed back to the shift register's inputs. When used as a test generation, an LFSR is about to cycle rapidly through an outsized number of its states. These states, whose choice and order depend upon the planning parameters of the LFSR, define the test patterns. during this mode of operation, an LFSR is seen as a source of (pseudo) random tests that are, in theory, applicable to any fault and circuit types. There are  $n$  flip-flops ( $X_{n-1}, \dots, X_0$ ) and this is called  $n$ -stage LFSR. It can be a near-exhaustive test pattern generator as it cycles through  $2^n - 1$  states excluding the zero state.



Standard LFSR model


## Output Response Compactor

There is huge amount of data involved in CUT response. It is uneconomical to store all these responses on the chip and compare during the BIST operation, therefore it is mandatory to compact responses before compaction. Large volume of response is compacted into a signature before comparison. The signature is stored on the chip. There are two approaches available.

1. In first approach we compact a single serial bit stream into a LFSR based compactor, called signature analyser.
2. In the second approach several bit streams are compacted into a special LFSR based compactor called multi-input signature register (MISR).
 
## MISR: Multiple-Input Signature Register

A serial-input signature register can only be used to test logic with a single output. The idea of a serial input signature register can be extended to multiple-input signature register (MISR). There are several ways to connect the inputs of LFSRs to form an MISR. Since the XOR operation is linear and associative,  $(A \text{ XOR } B) \text{ XOR } C = A \text{ XOR } (B \text{ XOR } C)$ , as long as the result of the additions are the same then the different representations are equivalent. If we have an  $n$ -bit long MISR we can accommodate up to  $n$  inputs to form the signature. If we use  $m < n$  inputs we do not need the extra XOR gates in the last  $n - m$  positions of the MISR. MISR reduce the amount of hardware required to compress a multiple bit stream. MISR circuit is implemented using a memory already existing in a circuit to be tested.



MISR model

## CUT (Circuit Under Test)

Circuit under test is a 4-bit Booth's Multiplier circuit. It is a very fast multiplication algorithm also capable of signed number multiplication. The Booth's algorithm the state machine used is described in the later sections.

Higher bit Booth's Multiplier can also be used, but to keep the testing simple, 4-bit Booth's Multiplier is used.

## LFSR and MISR used in the design


4-bit Booth's Multiplier has two inputs of 4-bit each. Hence a an LFSR capable of generating at least 8-bit pattern is required.

The output of 4-bit Booth's Multiplier is 8-bits, so there are 8 output patterns. So, at least 8-bit MISR is required for compaction.


An 8-bit internal XOR (type 2/ modular) LFSR and MISR of same characteristic polynomial is used in the design.

**Characteristic Polynomial:**  $x^8 + x^4 + x^3 + x^2 + 1$

 This is a **primitive polynomial**. It can generate all patterns from 1 to  $2^n-1$  exhibited by an 8-bit register except zero. Moreover, the Golden Section will be more unique when using a primitive polynomial MISR as compactor and probability of aliasing will also be minimal.



 
LFSR output pattern into *mc* (multiplicand) and *mp* (multiplier) of multiplier



*prod* output of multiplier into MISR compactor
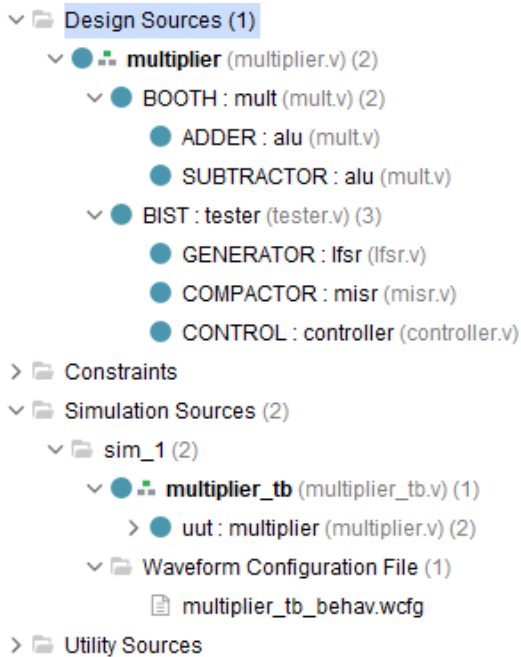
## Software Environment

The complete project is done in Xilinx Vivado Software Environment using Verilog as HDL. The various tools used include the text editor, Vivado Simulator, Synthesis and RTL Analysis. It is recommended to use the same software for evaluation purposes.



## The Design

Source code of the design is provided in the **Appendix A**. The top module consists of two sub modules, *mult* and *tester*. The design hierarchy is provided on the left.

When operating the multiplier in normal mode, the *tester* circuit is completely removed from the picture using multiplexers. Clock Gating technique is used when tester is not used to decrease the dynamic power.


When test mode is set, the I/O ports of multiplier is completely disconnected from user's control, and the tester gets invoked to control the multiplier and begin testing.

The whole circuit operates on two controllers, Booth's Algorithm Controller and BIST Controller. Hence there are two different state machines. In test mode, both the controller functions together by virtue of a **Handshaking Protocol** using various control signals between them.
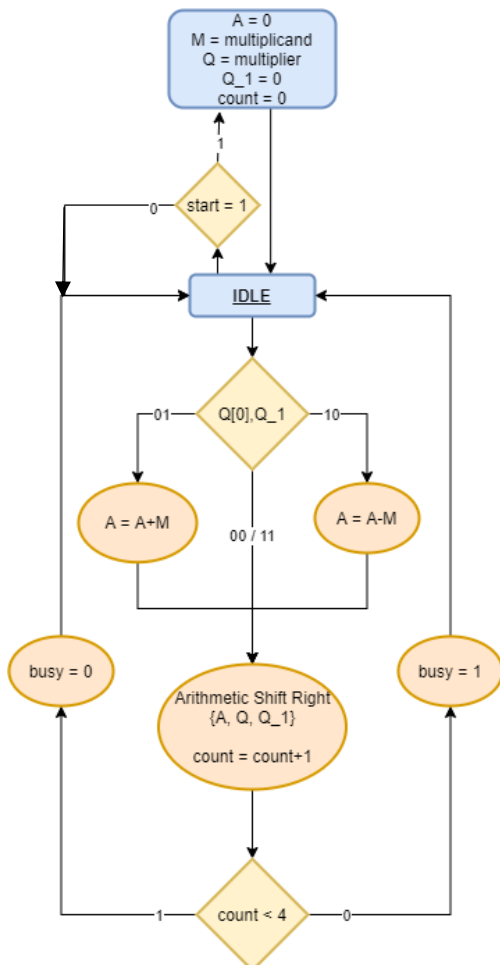
## Booth's Algorithm for Multiplier Circuit

- Initially the multiplier is in undefined state. On  $start = 1$ , the multiplier resets  $A$ ,  $Q\_1$  and  $count$  to zero.
- Next state is **Idle**, now the  $start$  signal needs to be zero otherwise it will again move to **reset state** and ask for parameters multiplier and multiplicand again.
- Check for  $\{Q[0], Q\_1\}$ . If  $\{0,1\}$  move to step 4, if  $\{1,0\}$  move to step 5, else skip to step 6.
- Assign  $A = A + M$ . Move to step 6.
- Assign  $A = A - M$ . Move to step 6.
- Arithmetic Shift Right, the triplet  $\{A, Q, Q\_1\}$ . Decrement  $count$ .
- Check for  $count < 4$ , if true set  $busy=0$  otherwise set  $busy=1$ . Move to **Idle** state and continue to step 3.

*Note: All of the steps from 3 to 7 are done in 1 clock cycle. It reduces the no. of states and increases the speed of FSM. But it may impose high timing constraints.*




## BIST Algorithm for tester circuit

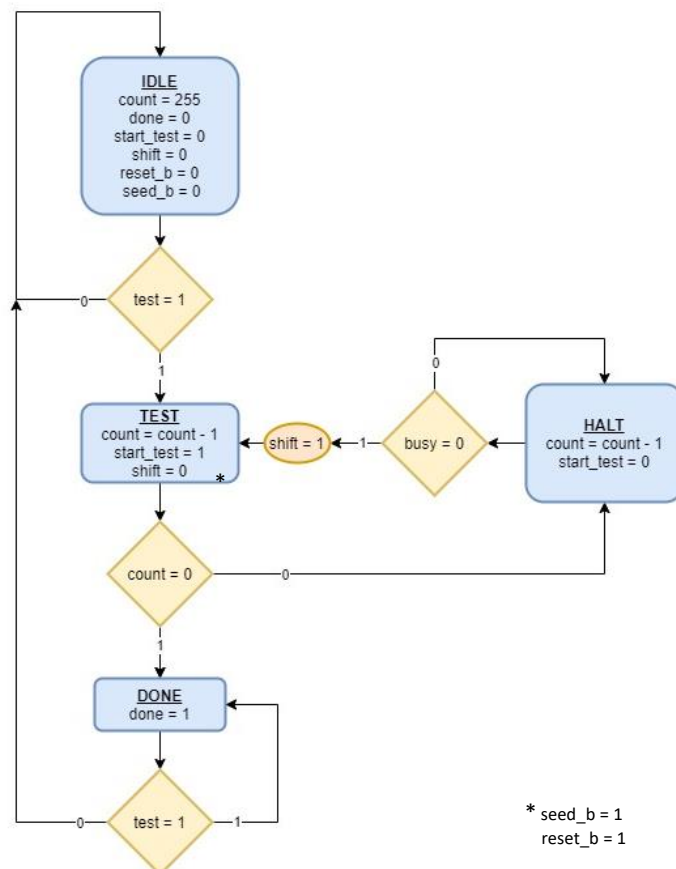
1. Reset all the signals to default zero value in **Idle State**. Reset to initial seed in LFSR and MISR to 1111\_1111 and 0000\_0000 by applying  $seed\_b = 0$  and  $reset\_b = 0$  respectively. The LFSR must be seeded to a non-zero value initially to generate pattern.
2. On  $test = 1$ , move to next state i.e. **Test State**. Issue  $start = 1$  on Booth's Multiplier. Set  $shift = 0$  to pause the pattern generator LFSR and compactor MISR. Set  $reset\_b$  and  $seed\_b$  as 1, as LFSR and MISR are already seeded.
3. If  $count = 0$  jump to step 4, else jump to step 6.
4. This is **Halt State**, the state machine remains in this state for most amount of time. Set the start  $signal = 0$  to begin multiplying.
5. If  $busy = 0$ , move to step 2 with  $shift = 1$  as mealy output. This signal resumes the LFSR generator and MISR compactor to shift and accept new values. Else stay in the current state.
6. This is **Done State**, the testing is completed hence set the  $done$  signal as 1.

After the test has been completed, the  $done$  signal is set to one and the obtained signature in MISR is compared with the valid signature, i.e.  $sign[7:0] = 0101\_1111B$  or **95D**. This valid signature can't be calculated manually, because test pattern polynomial is too large with maximum degree = 255. Hence the valid signature is obtained from the waveform in Vivado Simulator when there is not fault in the circuit. Later this signature is compared with the obtained signature in faulty circuit.


When the comparison is true, the  $pass$  signal is set 1 by the tester to indicate the circuit is not faulty.




## Top Module

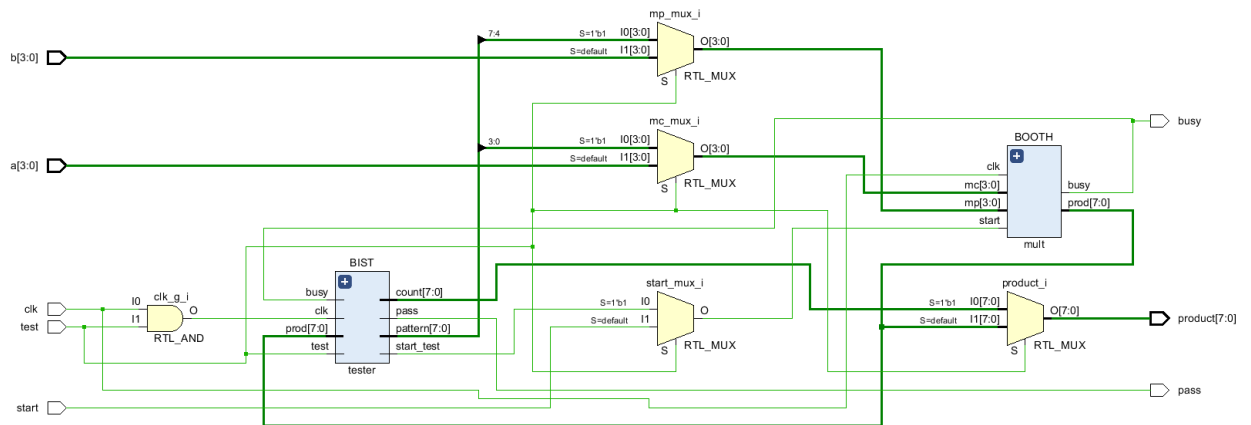

## Booth's Multiplier

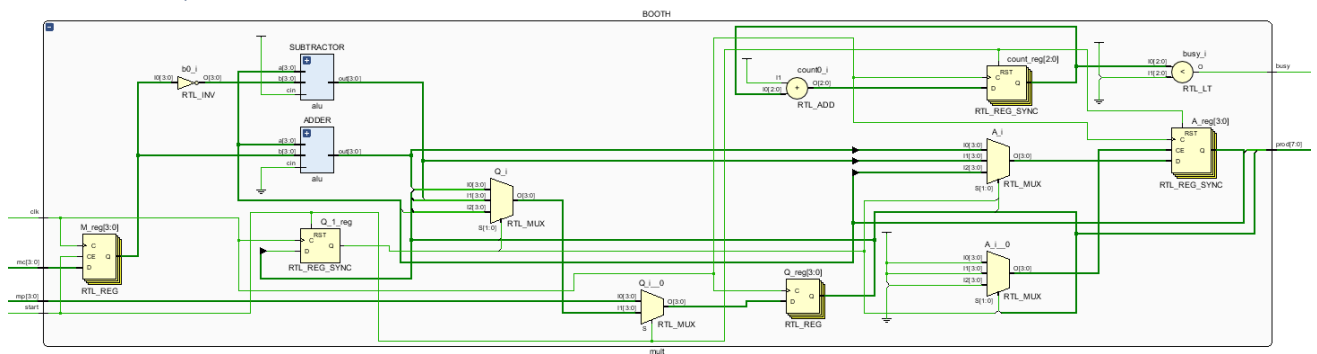


## BIST Tester

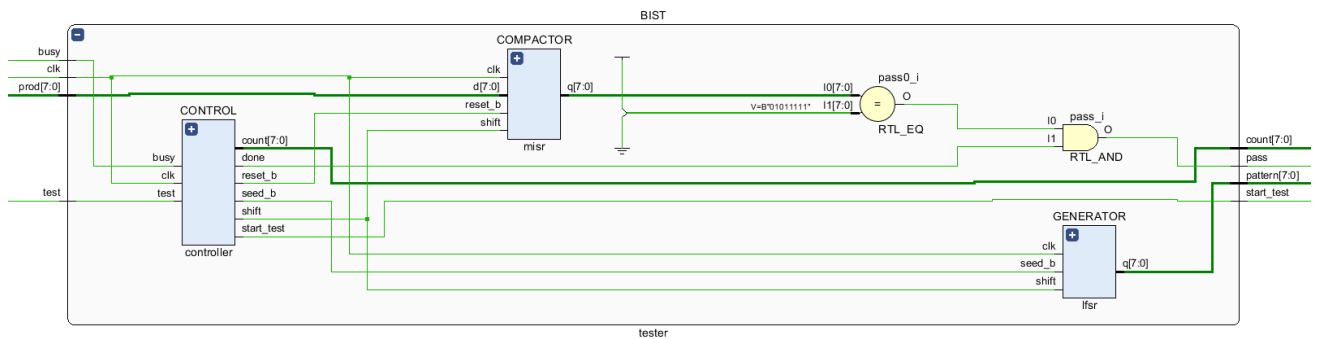



# Simulation Waveforms
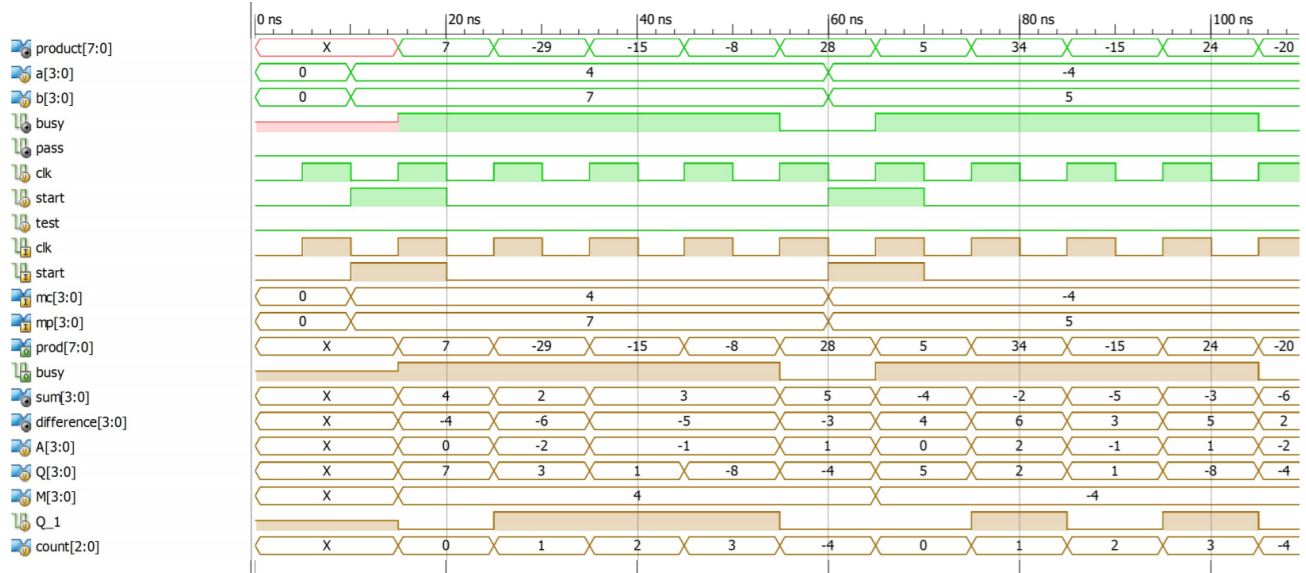
## Testbench waveform for Booth's Multiplier




Testbench code for above simulation can be found at **Appendix B1**. The signals in green are the i/o signals of the top UUT i.e. *multiplier*. The signals in golden are some important signals in the *mult* UUT. The inputs *a* and *b* are loaded with respective values and the *start* signal pulse is given to start the multiplication. Since the Booth's multiplier takes  $O(n)$  time units, where *n* is the type of Booth's Multiplier (here *n* = 4), hence the multiplication takes 40 ns to complete. In the while, the *busy* signal is set 1 to indicate the multiplication is not complete. Just after *busy* signal gets low, we get the desired product as result. The testbench also yields the following result in TCL Console.

```

1    product:    x busy: x at time=                    5000
2    first example: a = 4 b = 7
3    product:    7 busy: 1 at time=                    15000
4    product:   -29 busy: 1 at time=                    25000
5    product:   -15 busy: 1 at time=                    35000
6    product:    -8 busy: 1 at time=                    45000
7    product:   28 busy: 0 at time=                    55000
8    first example done
9    second example: a = -4 b = 5
10   product:    5 busy: 1 at time=                    65000
11   product:   34 busy: 1 at time=                    75000
12   product:  -15 busy: 1 at time=                    85000
13   product:   24 busy: 1 at time=                    95000
14   product:  -20 busy: 0 at time=                   105000
15   second example done

```
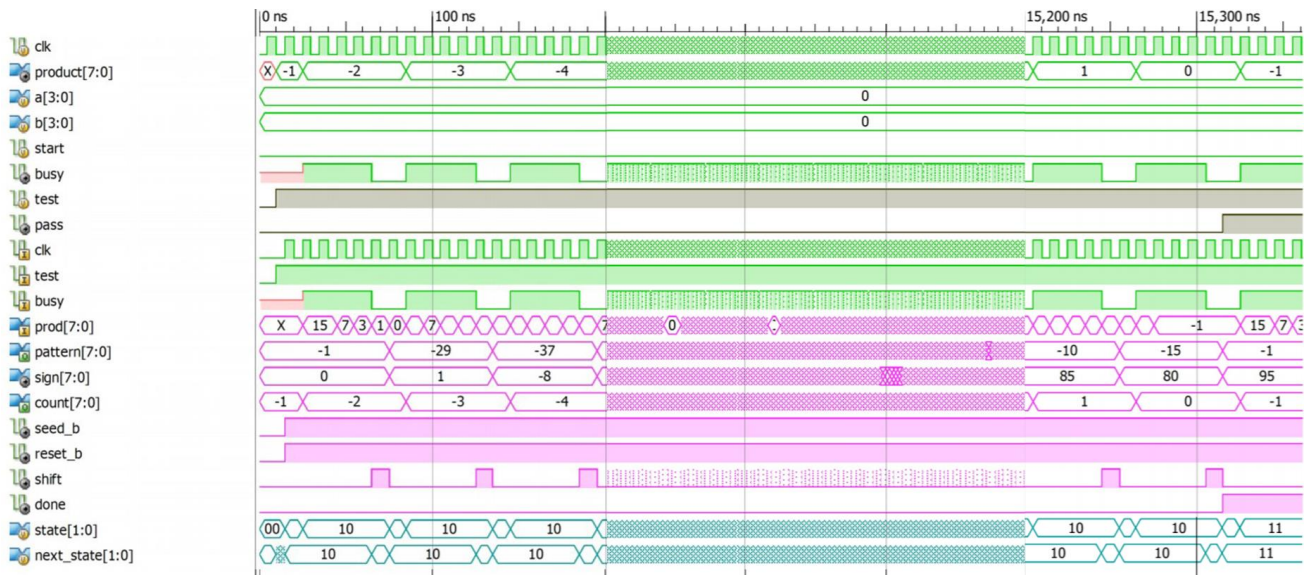
## Testbench waveform for BIST Tester Circuit with properly functioning Booth's Multiplier




Testbench code for above simulation can be found at **Appendix B2**. The signals in green are the i/o signals of the top UUT i.e. *multiplier*. The signals in pink are some important signals in the *tester* UUT. The signals in blue indicates state and next state of the BIST *Controller* UUT. The test and pass signals are colored grey to highlight them. When the test signal is high, the multiplier inputs and outputs are completely disconnected from user's control and are connected to the BIST tester. The tester follows the state machine described earlier. The output *product* signal is connected to *count* of the BIST controller. This provides an extra feature to display the time remaining for the test to complete to the user. The product signal down counts from 255 to 0 in (unsigned decimal form). When count value reaches 1111\_1111B or -1, it indicates the testing is complete. Since the *pass* signal is 1 in the waveform, this means the signature is matched with the valid signature and test is passed. The tester is reset when *test* = 0. Since same *mult* module is used in this testing purpose, it will obviously *show pass* = 1 whenever testing is complete, because no internal modification has been done in the *mult* module.

The time taken by this test to large for the waveform to fit in the report, hence the middle part of waveform has been shrunk to show to results.

Since there are  $2^n - 1$  total patterns generated by the LFSR generator (excluding pattern 0000\_0000B), the time taken to complete the test is approximately  $O(2^{2n} - 1)$  units, where  $n$  is the type of multiplier ( $n=4$  for 4 bit multiplier). Each multiplication takes  $O(n)$  time units. And in test mode, 2 more time units are required for state transition of BIST controller. Hence total time for test can be calculated by using formula  $(2^{2n} - 1)(n + 2)$  time units or  $(2^{2n} - 1)(n + 2) * 10$  ns for 100 MHz clock as used in the simulation or typical FPGA considering zero timing violations.

Time taken for test to complete for 4-bit Booth's Multiplier =  $(2^{2*4} - 1)(4 + 2) * 10$  ns = 15300 ns = 15.3  $\mu$ s
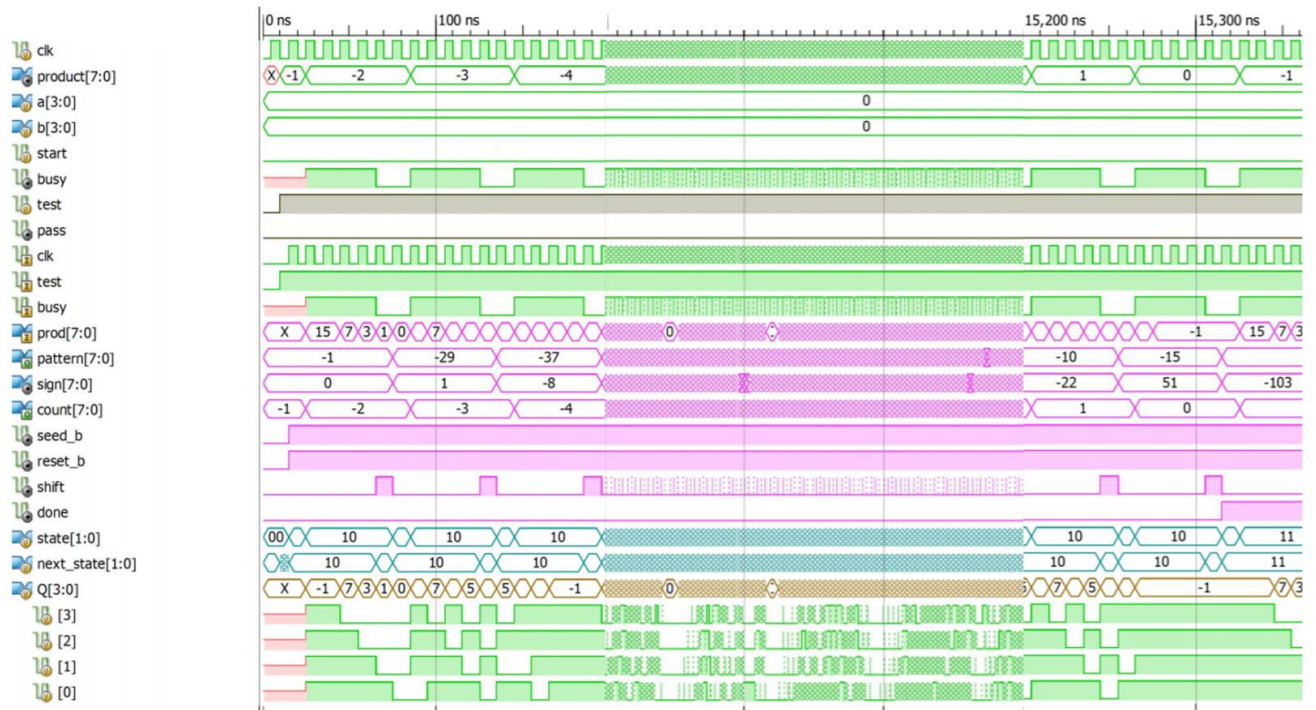
## Testbench waveform for BIST Tester Circuit with faulty Booth's Multiplier



Testbench code for above simulation can be found at **Appendix B3**. Using a normal testbench on the circuit will always show *pass* = 1 when testing using BIST feature, as the circuit is never faulty in frontend pre-production process. Hence the testbench in Appendix B3 is empty with no stimulus. Faults must be created in *mult* module intentionally. To create stuck-at-0 or stuck-at-1, any individual signals inside *mult* module can be forced to 0 or 1 respectively using Vivado Simulator GUI. This task can also be automated using TCL scripts in the console. The used TCL scripts for simulation provided in **Appendix C**. The signals in green are the i/o signals of the top UUT i.e. *multiplier*. The signals in pink are some important signals in the *tester* UUT. The signals in blue indicates *state* and *next state* of the BIST *Controller* UUT. The *test* and *pass* signals are colored grey to highlight them. At last, an extra signal *Q[3:0]* with golden colour is added to waveform. This signal shows the value of Q register in *mult* module. Modifying or forcing this signal will interfere with the results of the product and hence change the final signature. In this case the signal *Q[1]* is forced to stuck-at-1 from time interval 6020 ns to 6140 ns (just for 120 ns). The force is removed and then testbench is run normally.

The product signal is down counting as always. When BIST testing is complete the product signal reaches 0 and the shows 1111\_1111B or -1. At this moment the *pass* signal is still low, indicating that the circuit is faulty. The test takes same time (i.e. 15300 ns) to complete.

## Conclusions

### Probability of aliasing

It is the probability of that fault has occurred but not detected. It can be determined easily using the formula,

$$\text{Probability of aliasing} = 2^{-n} = 2^{-8} = 0.0039 \text{ (n = 8, size of Compactor)}$$

### Utilisation

The hardware overhead or utilization can be manually calculated by analysing the source code in **Appendix A**.

The BIST multiplier circuit consists of 3 registers (A, Q, M) contributing to  $3n$  FFs. The count register is sized  $(\log_2 n + 1)$ . One Q\_1 reg takes 1 FF more.

$$\text{Booth's Multiplier hardware utilisation (FF)} = 3n + (\log_2 n + 1) + 1 = 3n + \log_2 n + 2$$

Similarly, for tester circuit compactor and generator contributes to  $2*(2n)$  FFs. The counter in the controller needs  $2n$  FFs. Two more FFs are required for 4-states.

$$\text{BIST Tester hardware utilisation (FF)} = 2*(2n) + 2n + 2 = 6n + 2$$

$$\text{Total hardware utilisation (Booth + tester)} = (3n + \log_2 n + 2) + (6n + 2) = 9n + \log_2 n + 4$$

(for an n-bit Multiplier Circuit)

$$\text{Hardware (FF) utilisation without tester} = 3n + \log_2 n + 2 = 16$$

$$\text{Hardware (FF) utilisation without tester} = 9n + \log_2 n + 4 = 42 \quad (n = 4)$$

This can be verified using Utilization Reports from Vivado Synthesis Tool. The following table describes the utilization of various resources.

Resource	Utilization (without BIST)	Utilization (with BIST)	Times Increase
LUT	13	45	3.46x
FF	16	42	2.62x
IO	19	21	1.11x
BUFG	1	1	1.00x

IO and BUFG is irrelevant and LUTs can be assumed to be proportionate to FF consumption. This simplifies the calculation the hardware overhead for the tester.

Type of Multiplier	FF Utilization (without BIST)	FF Utilization (with BIST)	Times Increase
Booth 2-bit	9	23	2.55x
Booth 4-bit	16	45	2.81x
Booth 8-bit	29	79	2.72x
Booth 16-bit	54	152	2.81x
Booth 32-bit	103	297	2.88x

It can be concluded that incorporating BIST tester for a Booth's Multiplier will consume 2.7x more hardware resources. Hence percentage increase in resources almost remains constant with size of multiplier. Other parameters like static and dynamic power will also show similar characteristics.

### Test Duration

The test duration can be calculated using the previous formula derived in Simulation Section.

$$\text{Test Time} = (2^{2n} - 1) (n + 2) * 10 \text{ ns} \quad (\text{for } 100 \text{ MHz clock})$$

Type of Multiplier	Test Time	
	(ns)	(- units)
Booth 2-bit	600	600 ns
Booth 4-bit	15300	15.3 $\mu$ s
Booth 8-bit	6553500	6.55 ms
Booth 16-bit	$7.731 \times 10^{11}$	12 min 53 secs
Booth 32-bit	$6.172 \times 10^{21}$	195.7 millenniums

Hence it is very impractical to incorporate BIST testing beyond a 16-bit multiplier circuit.

## References

1. Hardware Modelling using Verilog, Prof-I. Sengupta, IT Kharagpur, NPTEL Courseware.
2. IJERT Special issue 2015, B. John and C. Mathew, Design and Implementation of Built in Self-Test (BIST) for VLSI circuit using Verilog
3. IEEE Design and Test of Computers, 1993, Vishwani D Agarwal, Charles R Kime, Kewal K Saluja-A Tutorial on Built-in Self-Test
4. <https://www.partow.net/programming/polynomials/index.html>
5. Testing and Diagnosis of Digital Design Class Notes.

## Source code and Testbenches

Although, the source code and testbenches are provided in the Appendix Section. For evaluation or prototyping purposes, it is recommended to import the codes from the following GitHub Repository to prevent any syntax errors.

<https://github.com/avisekh007/booth-multiplier-bist>

## APPENDIX A: SOURCE CODE

### Top Module (multiplier)

```
1  module multiplier(
2      input clk,
3      input [3:0] a, b,
4      input start, test,
5      output [7:0] product,
6      output busy, pass
7  );
8
9      wire [3:0] mc_mux, mp_mux;
10     wire [7:0] pattern, count, prod;
11
12     // Booth's Multiplier Module
13     mult BOOTH (
14         .clk(clk),
15         .start(start_mux),
16         .mc(mc_mux),
17         .mp(mp_mux),
18         .prod(prod),
19         .busy(busy)
20     );
21
22     // Built-in Self-Test Module
23     tester BIST (
24         .clk(clk_g),
25         .test(test),
26         .busy(busy),
27         .prod(prod),
28         .start_test(start_test),
29         .pass(pass),
30         .pattern(pattern),
31         .count(count)
32     );
33
34     // If test=1, connect the tester module to the mult module
35     assign mc_mux    = (test) ? pattern[3:0] : a,
36            mp_mux    = (test) ? pattern[7:4] : b,
37            start_mux = (test) ? start_test  : start,
38            product   = (test) ? count      : prod;
39
40     assign clk_g = clk && test; //clock gating to reduce dynamic power dissipation when
41     tester is not in use
42
43 endmodule
```

## Booth's Multiplier and ALU

```
1  module mult(
2      input clk, start,
3      input [3:0] mc, mp, //multiplicand and multiplier
4      output [7:0] prod, //product
5      output busy //when busy=1, result is not ready
6  );
7
8      reg [3:0] A, Q, M;
9      reg Q_1;
10     reg [2:0] count;
11     wire [3:0] sum, difference;
12
13     always @(posedge clk) begin
14         if(start) begin //reset all registers and initialise M and Q on start
15             A <= 4'b0;
16             M <= mc;
17             Q <= mp;
18             Q_1 <= 1'b0;
19             count <= 3'b0;
20         end
21
22         else begin
23             case({Q[0], Q_1}) //Booth's Algorithm
24                 2'b0_1 : {A, Q, Q_1} <= {sum[3], sum, Q}; //arithmetic shift left {A, Q, Q_1}
25                 2'b1_0 : {A, Q, Q_1} <= {difference[3], difference, Q};
26                 default: {A, Q, Q_1} <= {A[3], A, Q};
27             endcase
28             count <= count + 1'b1;
29         end
30     end
31
32     // Instantiation of alu as adder and subtractor
33     alu ADDER (A, M, 1'b0, sum);
34     alu SUBTRACTOR (A, ~M, 1'b1, difference);
35
36     assign prod = {A, Q};
37     assign busy = (count < 4); //4-bit multiplier completes the operation on 4th count,
38     //make busy low on 4th count
39
40 endmodule
41
42 /* ALU as an adder, but capable of subtraction:
43    Subtraction means adding the two's complement,
44    a - b = a + (-b) = a + (inverted b + 1)
45    The 1 will be coming in as cin (carry-in) */
46
47 module alu(
48     input [3:0] a, b,
49     input cin,
50     output [3:0] out
51 );
52
53     assign out = a + b + cin;
54
55 endmodule
```

## BIST Tester Top Module

```
1  module tester(  
2      input clk,  
3      input test, busy,  
4      input [7:0] prod,  
5      output start_test, pass,  
6      output [7:0] pattern, count  
7  );  
8  
9      wire [7:0] sign;  
10  
11     //Input Pattern Genarator  
12     lfsr GENERATOR (  
13         .clk(clk),  
14         .seed_b(seed_b),  
15         .shift(shift),  
16         .q(pattern)  
17     );  
18  
19     //Output Response Compactor  
20     misr COMPACTOR (  
21         .clk(clk),  
22         .reset_b(reset_b),  
23         .shift(shift),  
24         .d(prod),  
25         .q(sign)  
26     );  
27  
28     controller CONTROL (  
29         .clk(clk),  
30         .test(test),  
31         .busy(busy),  
32         .seed_b(seed_b),  
33         .reset_b(reset_b),  
34         .shift(shift),  
35         .start_test(start_test),  
36         .done(done),  
37         .count(count)  
38     );  
39  
40     assign pass = (sign == 8'b0101_1111) && done;  
41     //Signature is compared with the valid one when the testing is complete.  
42  
43 endmodule
```



## LFSR Pattern Generator and MISR Response Compactor

```
1  module lfsr(  
2      input clk, seed_b, shift,  
3      output reg [7:0] q  
4  );  
5  
6      //Characteristic Polynomial :  $x^8 + x^4 + x^3 + x^2 + 1$   
7      always @(posedge clk, negedge seed_b) begin  
8          if(~seed_b)  
9              q <= 8'b1111_1111; //initial seed != 0  
10         else if(shift) begin  
11             q[0] <= q[7];  
12             q[1] <= q[0];  
13             q[2] <= q[1]^q[7];  
14             q[3] <= q[2]^q[7];  
15             q[4] <= q[3]^q[7];  
16             q[5] <= q[4];  
17             q[6] <= q[5];  
18             q[7] <= q[6];  
19         end  
20     end  
21  
22 endmodule
```

```
1  module misr(  
2      input clk, reset_b, shift,  
3      input [7:0] d,  
4      output reg [7:0] q  
5  );  
6  
7      //Characteristic Polynomial :  $x^8 + x^4 + x^3 + x^2 + 1$   
8      always @(posedge clk, negedge reset_b) begin  
9          if(~reset_b)  
10             q <= 8'b0; //initial seed = 0  
11         else if(shift) begin  
12             q[0] <= q[7]^d[0];  
13             q[1] <= q[0]^d[1];  
14             q[2] <= q[1]^q[7]^d[2];  
15             q[3] <= q[2]^q[7]^d[3];  
16             q[4] <= q[3]^q[7]^d[4];  
17             q[5] <= q[4]^d[5];  
18             q[6] <= q[5]^d[6];  
19             q[7] <= q[6]^d[7];  
20         end  
21     end  
22  
23  
24 endmodule
```

## BIST Controller

```
1  module controller(
2      input clk,
3      input test, busy,
4      output reg seed_b, reset_b, shift,
5      output reg start_test, done,
6      output reg [7:0] count
7  );
8
9      parameter IDLE = 2'b00, // not testing
10         TEST = 2'b01, // multiplier ready
11         HALT = 2'b10, // multiplier not ready
12         DONE = 2'b11; // testing finished
13
14      reg [1:0] state, next_state;
15
16      always @(posedge clk, negedge test) begin
17          if (~test) begin // disable testing on test signal low
18              state <= IDLE;
19              count <= 255; // 2^8-1 = 255 combinations of pattern to be checked
20          end
21          else begin
22              state <= next_state;
23              if(state == TEST) count <= count - 1'b1; // decrease count on every sucessful compaction
24          end
25      end
26
27      // next-state combinational logic
28      always @(*) begin
29          next_state = state;
30          case (state)
31              IDLE : if(test) next_state = TEST;
32              TEST : begin
33                  if(count==0) next_state = DONE; // finish testing when all 255 combinatons of pattern
34                  are checked
35                  else next_state = HALT; // halt and wait for multiplier to get ready
36              end
37              HALT : if(busy==0) next_state = TEST; // resume testing when multiplier is ready
38          endcase
39      end
40
41      // output combinational logic
42      always @(*) begin
43          reset_b = 1'b1; // default value for all control signals
44          seed_b = 1'b1;
45          done = 1'b0;
46          start_test = 1'b0;
47          shift = 1'b0;
48
49          case (state)
50              IDLE : begin
51                  reset_b = 1'b0;
52                  seed_b = 1'b0;
53              end
54              TEST : start_test = 1'b1; // start testing as multilprier is ready
55              HALT : if(busy==0) shift = 1'b1; // shift LFSR & MISR when multiplier operation is finished
56              DONE : done = 1'b1; // indicates testing is finished
57          endcase
58      end
59  endmodule
```

## Appendix B: Testbench Code

### B1: Testbench for normal multiplier functionality

```
1  `timescale 1ns / 1ps
2
3  module multiplier_tb;
4
5      // Inputs
6      reg clk;
7      reg [3:0] a;
8      reg [3:0] b;
9      reg start;
10     reg test;
11
12     // Outputs
13     wire [7:0] product;
14     wire busy;
15     wire pass;
16
17     // Instantiate the Unit Under Test (UUT)
18     multiplier uut (
19         .clk(clk),
20         .a(a),
21         .b(b),
22         .start(start),
23         .test(test),
24         .product(product),
25         .busy(busy),
26         .pass(pass)
27     );
28
29     always #5 clk = ~clk;
30
31     always @(posedge clk) $strobe("product: %d busy: %d at time=%t", $signed(product),
32     busy, $stime);
33
34     initial begin
35         // Initialize Inputs
36         clk = 0;
37         a = 0;
38         b = 0;
39         start = 0;
40         test = 0;
41         // Add stimulus here
42
43         #10;
44         $display("first example: a = 4 b = 7");
45         a = 4; b = 7; start = 1; #10 start = 0;
46         #40 $display("first example done");
47         $display("second example: a = -4 b = 5");
48         a = -4; b = 5; start = 1; #10 start = 0;
49         #40 $display("second example done");
50         $finish;
51     end
52
53 endmodule
```

## B2: Testbench for Tester Circuit with properly functioning Booth's Multiplier

```
1  `timescale 1ns / 1ps
2
3  module multiplier_tb;
4
5      // Inputs
6      reg clk;
7      reg [3:0] a;
8      reg [3:0] b;
9      reg start;
10     reg test;
11
12     // Outputs
13     wire [7:0] product;
14     wire busy;
15     wire pass;
16
17     // Instantiate the Unit Under Test (UUT)
18     multiplier uut (
19         .clk(clk),
20         .a(a),
21         .b(b),
22         .start(start),
23         .test(test),
24         .product(product),
25         .busy(busy),
26         .pass(pass)
27     );
28
29     always #5 clk = ~clk;
30
31     initial begin
32         // Initialize Inputs
33         clk = 0;
34         a = 0;
35         b = 0;
36         start = 0;
37         test = 0;
38         // Add stimulus here
39
40         #10;
41         test = 1;
42
43         #100;
44         wait(product == 8'b1111_1111);
45
46         #10;
47         if(pass == 1)
48             $display("Test Passed!");
49         else
50             $display("Test Failed!");
51
52         #30;
53         test = 0;
54
55     $finish;
56
57     end
58
59 endmodule
```

### B3: Testbench for Tester Circuit with faulty Booth's Multiplier

```
1  `timescale 1ns / 1ps
2
3  module multiplier_tb;
4
5      // Inputs
6      reg clk;
7      reg [3:0] a;
8      reg [3:0] b;
9      reg start;
10     reg test;
11
12     // Outputs
13     wire [7:0] product;
14     wire busy;
15     wire pass;
16
17     // Instantiate the Unit Under Test (UUT)
18     multiplier uut (
19         .clk(clk),
20         .a(a),
21         .b(b),
22         .start(start),
23         .test(test),
24         .product(product),
25         .busy(busy),
26         .pass(pass)
27     );
28
29     always #5 clk = ~clk;
30
31     initial begin
32         // Initialize Inputs
33         clk = 0;
34         a = 0;
35         b = 0;
36         start = 0;
37         test = 0;
38         // Add stimulus here
39     end
40
41 endmodule
```

## Appendix C: TCL Commands for forcing multiplier to behave faulty

```
1 restart
2 run 10 ns
3 add_force {/multiplier_tb/test} -radix bin {1 1ps}
4 run 10 ns
5 run 6000 ns
6 add_force {/multiplier_tb/uut/BOOTH/Q[1]} -radix bin {1 1ps}
7 run 60 ns
8 run 60 ns
9 remove_forces { {/multiplier_tb/uut/BOOTH/Q[1]} }
10 run 60 ns
11 run 60 ns
12 run 9120 ns
13 add_force {/multiplier_tb/test} -radix bin {0 1ps}
14 run 60 ns
```